

WARNING

This material has been reproduced and communicated to you by or on behalf of *Charles Darwin University* in accordance with section 113P of the *Copyright Act 1968 (Act)*.

The material in this communication may be subject to copyright under the Act.
Any further reproduction or communication of this material by you may be the subject of copyright protection under the Act.

Do not remove this notice



Family Name	
Given Names	
Student Number	
Teaching Period	Semester 1, 2017

FINAL EXAMINATION	DURATION
ENG221 – Analogue Electronics	Reading Time: 10 minutes
	Writing Time: 180 minutes

INSTRUCTIONS TO CANDIDATES

EXAM CONDITIONS

You may begin writing from the commencement of the examination session. The reading time indicated above is provided as a guide only.

- This is a CLOSED BOOK examination
- Any non-programmable calculator is permitted
- No handwritten notes are permitted
- No dictionaries are permitted


ADDITIONAL AUTHORISED MATERIALS	EXAMINATION MATERIALS TO BE SUPPLIED
none	1 x 20 Page Book 1 x Scrap Paper Formula Sheet/s

**THIS EXAMINATION IS PRINTED
DOUBLE-SIDED.**

**THIS PAGE HAS BEEN INTENTIONALLY LEFT
BLANK.**

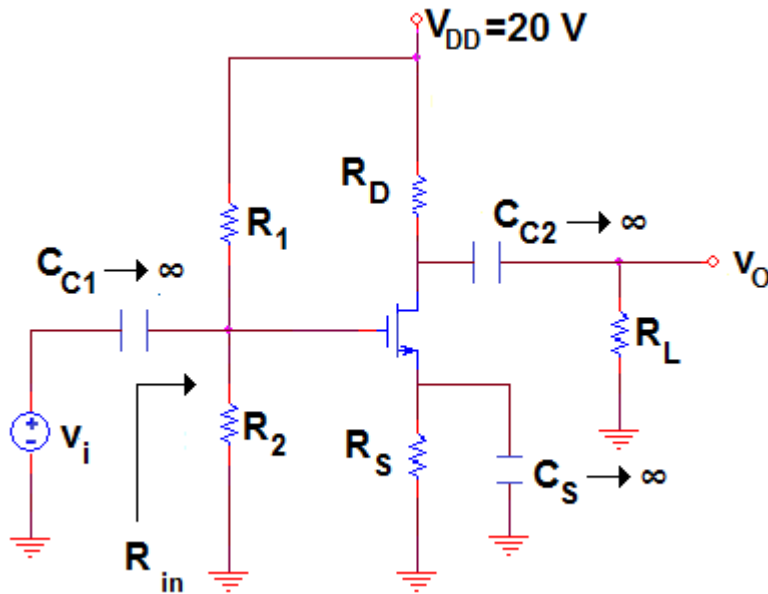Question 1 (20 marks)

For the amplifier shown in Figure 1, design the circuit (by determining values of R_1 , R_2 , R_D and R_S) to achieve a small-signal voltage gain of at least $A_v = -10$ V/V for $R_L = 20$ k Ω and $R_{in} = 200$ k Ω . Assume that the transistor operates at $I_D = 1$ mA and $V_{DS} = 10$ V. Let $V_t = 2$ V and $\lambda = 0$.



Neamen, 3rd edition, 978-0073285962


Figure 1.

Question 2 (15 marks)

For the circuit shown in Figure 2, answer the following questions:

- Determine the value of R_S such that $I_D = 5 \text{ mA}$. (4 marks)
- Based on the results obtained from part (a), determine the small-signal voltage gain ($A_v = v_o/v_i$). (8 marks)
- Based on the results obtained from part (a), determine the output resistance (R_o). (3 marks)

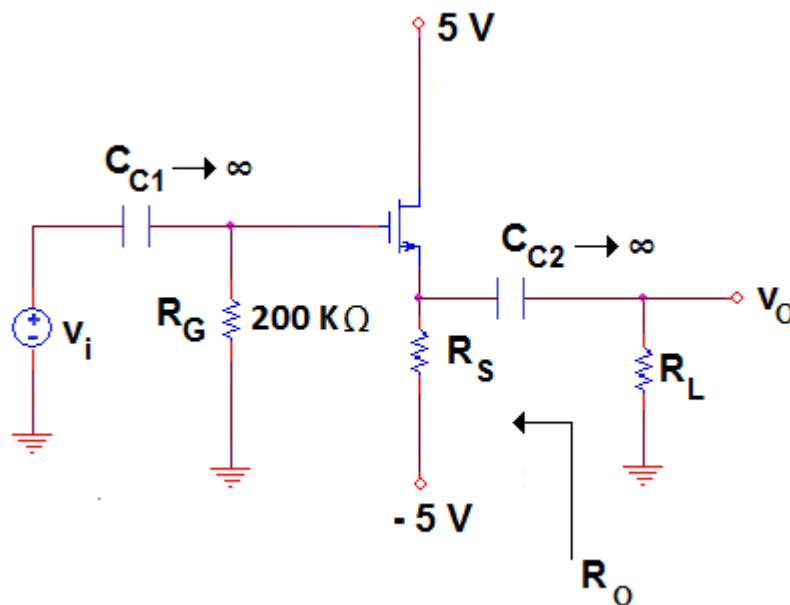Assume $R_L = 2 \text{ k}\Omega$. The transistor's parameters are $V_t = 2 \text{ V}$, $K'_n(W/L) = 2 \text{ mA/V}^2$ and $\lambda = 0.01 \text{ V}^{-1}$.




Neamen, 3rd edition, 978-0073285962

Figure 2.

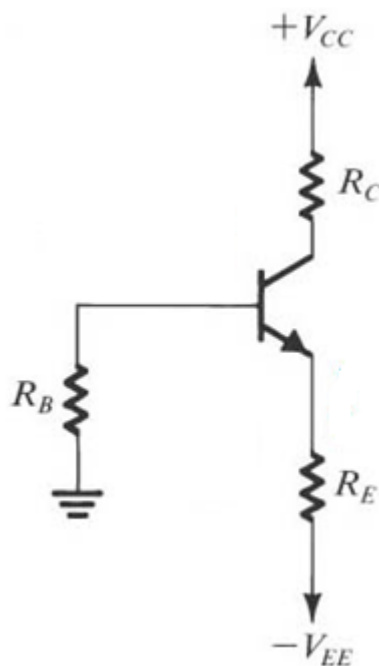Question 3 (15 marks)

Consider the circuit shown in Figure 3, which is supplied by ± 3 Volts. It is required to design the circuit so that $I_C = 3$ mA and V_C is placed midway between V_{CC} and V_E .

- For $\beta = \infty$, what values of R_E and R_C are required? (5 marks)
- If the transistor is specified to have a minimum β of 90, determine the largest value for R_B consistent with the need to limit the voltage drop across it to one-tenth the voltage drop across R_E . (5 marks)
- Based on results obtained from part (b), what are values of R_E and R_C ? (5 marks)




Sedra, 6th edition, ISBN: 9780199738519

Figure 3.

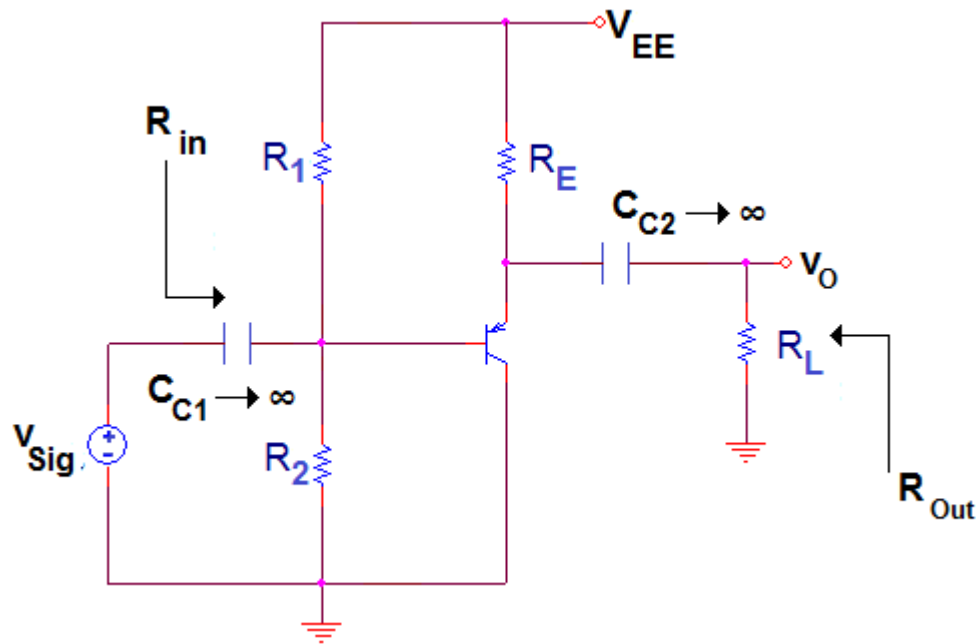Question 4 (15 marks)

For the circuit shown in Figure 4, let $V_{EE}=5\text{ V}$, $R_L=4\text{ K}\Omega$, $R_E=3\text{ K}\Omega$, $R_1=60\text{ K}\Omega$, and $R_2=40\text{ K}\Omega$. The transistor's parameters are $\beta=50$ and $V_A=80\text{ V}$.

- Determine the quiescent point of the transistor (I_E and V_{EC}). (5 marks)
- Determine the overall voltage gain $A_V=v_o/v_{sig}$. (4 marks)
- Determine the input resistance (R_{in}). (3 marks)
- Determine the output resistance (R_{out}). (3marks)



Neamen, 3rd edition, 978-0073285962


Figure 4.

Question 5 (25 marks)

In the circuit shown in Figure 5,

- Determine the collector current of the transistor. (6 marks)
- Using either the π or the T model, determine the overall voltage gain (v_o/v_{sig}). (8 marks)
- Using either the π or the T model, determine the input resistance (R_i). (6 marks)
- Using either the π or the T model, determine the output resistance (R_{out}). (5 marks)

Assume that $\beta=80$ and $\lambda=0$.

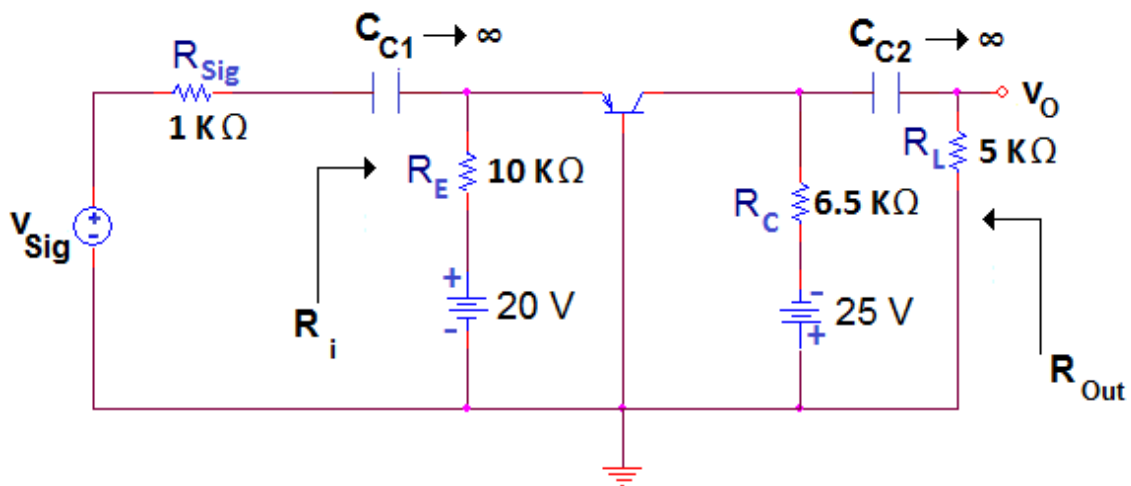

Neamen, 3rd edition, 978-0073285962

Figure 5.

Formula sheet

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \left(1 + \frac{v_{DS}}{V_A}\right) = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \left(1 + \frac{v_{DS}}{V_A}\right)$$

NMOSFET

$$g_m = (\mu_n C_{ox}) \left(\frac{W}{L}\right) V_{OV} = \sqrt{2(\mu_n C_{ox}) \left(\frac{W}{L}\right) I_D}$$

$$r_o = \frac{V_A}{I_D}$$

$$V_A = \frac{1}{\lambda} \quad g_m = \frac{I}{V_{OV}/2}$$

PMOSFET

$$i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{SG} - |V_t|)^2 \left(1 + \frac{v_{SD}}{V_A}\right) = \frac{1}{2} k'_p \frac{W}{L} (v_{SG} - |V_t|)^2 \left(1 + \frac{v_{SD}}{V_A}\right)$$

$$g_m = (\mu_p C_{ox}) \left(\frac{W}{L}\right) V_{OV} = \sqrt{2(\mu_p C_{ox}) \left(\frac{W}{L}\right) I_D}$$

$$r_o = \frac{|V_A|}{I_D}$$

$$V_A = \frac{1}{\lambda}$$

BJT

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$i_B = \frac{i_C}{\beta} \quad \Delta I_B = \frac{\Delta I_C}{\beta}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m r_e = \alpha$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$r_\pi = \frac{\beta}{g_m}$$

$$r_o = \frac{V_A}{I_C}$$

$$V_T = 25 \text{ mV} \quad V_{BE} = 0.7 \text{ V}$$