

WARNING

This material has been reproduced and communicated to you by or on behalf of *Charles Darwin University* in accordance with section 113P of the *Copyright Act 1968 (Act)*.

The material in this communication may be subject to copyright under the Act.
Any further reproduction or communication of this material by you may be the subject of copyright protection under the Act.

Do not remove this notice



Family Name					
Given Name/s					
Student Number					
Teaching Period	Semester 1, 2019				

ENG424 – Power Engineering	DURATION	
	Reading Time:	10 minutes
	Writing Time:	180 minutes
INSTRUCTIONS TO CANDIDATES		
<ol style="list-style-type: none"> 1. This examination is worth 50% of the total assessment for this unit. 2. Read the questions carefully before attempting. 3. Attempt all questions. Questions are not of equal value. 4. In order to explain your work, draw suitable (circuit) diagrams whenever possible. 5. Highlight the final answers. 6. Don't forget the units. Absence of a unit may cost you some credit. 		
EXAM CONDITIONS		
<u>You may begin writing from the commencement of the examination session.</u> The reading time indicated above is provided as a guide only.		
This is a CLOSED BOOK examination		
Any non-programmable calculator is permitted		
No handwritten notes are permitted		
No dictionaries are permitted		
ADDITIONAL AUTHORISED MATERIALS	EXAMINATION MATERIALS TO BE SUPPLIED	
No additional printed material is permitted	1 x 20 Page Book 1 x Scrap Paper	

**THIS EXAMINATION IS PRINTED
DOUBLE-SIDED.**

**THIS PAGE HAS BEEN INTENTIONALLY
LEFT BLANK.**

QUESTION 1 (15 MARKS)

Briefly answer the following questions.

- Q1.1** What is flux linkage? What is its unit? Use plain English, not equations. **(1 mark)**
- Q1.2** What is a power station? **(1 mark)**
- Q1.3** Power factor is the ratio of two quantities. What are they? **(1 mark)**
- Q1.4** How does a power transformer differ from a current or potential transformer? **(1 mark)**
- Q1.5** Power utilities around the world generate ac voltage in sinusoidal form. Why? **(1 mark)**
- Q1.6** Consider the numbers 1, 4, 13, 0, -3 and -7. Determine their root mean square value. **(1 mark)**
- Q1.7** What is the difference between core type and shell type transformers? **(1 mark)**
- Q1.8** What is eddy current loss in a transformer? Where does it occur? **(1 mark)**
- Q1.9** Do you also have eddy current losses in other machines such as induction motors and dc motors? **(1 mark)**
- Q1.10** Consider a 5A ammeter is connected to the secondary side of a 100/5A current transformer (CT) in order to measure the current of the circuit. Safety considerations require that the CT has to be short circuited (or the primary circuit switched off) during a replacement of the ammeter. Explain why this is needed. **(1 marks)**
- Q1.11** In a balanced three phase system, the magnitude of the line-to-line voltages roughly equal 1.732 times the magnitude of the phase voltages. Prove this statement by using a phasor diagram. **(2 marks)**
- Q1.12** What is root mean square value of a sinusoidal voltage? Prove that this is roughly 70.7% of its maximum value. **(3 marks)**

GO TO THE NEXT PAGE FOR QUESTION 2

QUESTION 2 (15 MARKS)

A single-phase power system is shown in Figure 2 below. The power source feeds a 100-kVA, 14/2.4-kV transformer through a feeder impedance of $38.2 + j 140$ ohms. The transformer equivalent series impedance referred to the low voltage side is $0.10 + j 0.40$ as shown. The load on the transformer is 90 kW at a lagging power factor of 0.8 and at a voltage of 2400 volts.

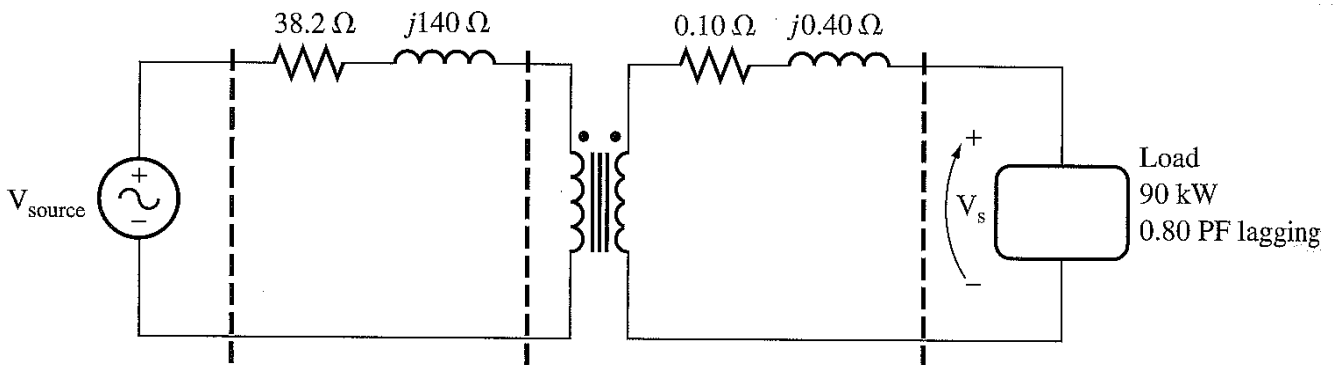


Figure 2: A simple power system for the Question 2.

- Q2.1** What will be the voltage at the source. **(10 marks)**
- Q2.2** What will be the voltage regulation of the transformer? **(3 marks)**
- Q2.3** What is the efficiency of the power system? **(2 marks)**

QUESTION 3 (10 MARKS)

When a 50-kVA, 3-phase, 440-volt, 60 Hz synchronous generator is driven at its rated speed, it is found that the open circuit terminal voltage is 440 volts line-to-line with a field current of 7 amps. When the stator terminals are shorted together, rated current is produced by a field current of 5.5 amps.

- Q3.1** Calculate the synchronous reactance of the machine. **(8 mark)**
- Q3.2** Calculate the synchronous reactance in per unit based on machine ratings. **(2 mark)**

QUESTION 4 (10 MARKS)

Write short notes on the following machines. **(2 marks each)**

- Q4.1** Universal motors
- Q4.2** Brushless DC machines
- Q4.3** Stepper motors
- Q4.4** Capacitor start motors
- Q4.5** Wound-rotor motors

FORMULAS

(Symbols have their usual meanings in the context of the particular formula)

MAGNETIC CIRCUITS

$$L = \lambda/i = N^2/\mathfrak{R} = \mu N^2 A/d;$$

$$Ni = \sum H\lambda = \phi \mathfrak{R}; \quad B = \mu H = \mu Ni/\lambda; \quad \mu = \mu_r \mu_0; \quad \mathfrak{R} = \lambda/\mu A$$

TRANSFORMERS

$$\frac{V_p(t)}{V_s(t)} = \frac{I_s(t)}{I_p(t)} = \frac{N_p}{N_s} = a; \quad Z'_2 = a^2 Z_2; \quad R'_c = \frac{V_{oc}}{I_{oc} \cos\theta}; \quad X'_m = \frac{V_{oc}}{I_{oc} \sin\theta}; \quad \cos\theta = \frac{P_{oc}}{V_{oc} I_{oc}};$$

$$\eta = \frac{P_{OUT}}{P_{IN}} = \frac{V_s I_s \cos(\theta_s)}{V_s I_s \cos(\theta_s) + P_{CORE} + P_{CU}} \times 100\%$$

$$\eta_{AD} = \frac{\text{Energy output over 24 hours}}{\text{Energy input over 24 hours}} \times 100\%$$

$$\text{Voltage Regulation} = \frac{|V_{S,NL}| - |V_{S,FL}|}{|V_{S,FL}|} \times 100\%$$

MACHINE FUNDAMENTALS

$$\mathbf{T} = \mathbf{r} \times \mathbf{F}; \quad \mathbf{F} = i(\boldsymbol{\ell} \times \mathbf{B}); \quad \mathbf{e}_{ind} = (\mathbf{v} \times \mathbf{B}) \cdot \boldsymbol{\ell}; \quad E_A = 4.44 f N \phi_{max}$$

ALTERNATORS

$$e = \frac{d\lambda}{dt} = L \frac{di}{dt}$$

$$E_f \propto I_f \quad E_f = V_t + I_a R_a + j I_a X_s \quad E_f = V_t + I_a R_a + j I_d X_d + j I_q X_q$$

$$P_{CONV}; \quad P_{OUT} = \frac{3 V_\phi E_A \sin(\delta)}{X_s}; \quad \tau_{ind} = \frac{3 V_\phi E_A \sin(\delta)}{\omega_m X_s}$$

$$P = \frac{|V_t| |E_f|}{|Z_s|} \cos(\theta_s - \delta) - \frac{|V_t|^2}{|Z_s|} \cos\theta_s \quad Q = \frac{|V_t| |E_f|}{|Z_s|} \sin(\theta_s - \delta) - \frac{|V_t|^2}{|Z_s|} \cos\theta_s$$

$$E_f = V_t \cos\delta \pm I_d X_d, \quad I_a = |I_q| - j |I_d| \quad \text{and} \quad V_t = |V_t| \angle -\delta$$

$$P = \frac{|V_t| |E_f|}{|X_d|} \sin\delta + \frac{|V_t|^2 (X_d - X_q)}{2 X_d X_q} \sin 2\delta \quad Q = \frac{|V_t| |E_f|}{|X_d|} \cos\delta + |V_t|^2 \left[\frac{\sin^2\delta}{X_q} + \frac{\cos^2\delta}{X_d} \right]$$

INDUCTION MACHINES

(Torque and power are given on a per phase basis)

$$n = 120 \frac{f}{p}; \quad f_2 = sf_1; \quad E_{\text{rms}} = 4.44f N_{\text{ph}} \phi_p K_w$$

$$\text{slip, } s @ \frac{n_{\text{slip}}}{n_{\text{sync}}} = \frac{n_{\text{sync}} - n_m}{n_{\text{sync}}} = 1 - \frac{n_m}{n_{\text{sync}}}$$

$$V_{TH} = V_\phi \frac{jX_M}{R_1 + j(X_1 + X_M)}; \quad Z_{TH} = R_{TH} + jX_{TH} = \frac{jX_M(R_1 + jX_1)}{R_1 + j(X_1 + X_M)}; \quad \tau_{\text{ind}} = \frac{3}{\omega_{\text{sync}}} I_2^2 \left(\frac{R_2}{s} \right);$$

$$\tau_{\text{ind}} = \frac{3V_{TH}^2}{\omega_{\text{sync}}} \frac{R_2/s}{(R_{TH} + R_2/s)^2 + (X_{TH} + X_2)^2} \quad S_{\text{max}} = \frac{R_2}{\sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}$$

$$\tau_{\text{max}} = \frac{3V_{TH}^2}{2\omega_{\text{sync}} \left[R_{TH} + \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2} \right]}$$

$$P_{\text{mech}} = T_{\text{mech}} \omega_{\text{mech}} = (1-s)P_{\text{air_gap}}; \quad \text{Ideal Efficiency} = 1-s;$$

$$T_{\text{mech}} = \frac{1}{\omega_s} I_2'^2 \frac{R_2'}{s} = \frac{1}{\omega_s} \frac{V_{\text{th}}^2}{(R_{\text{th}} + R_2'/s)^2 + (X_{\text{th}} + X_2')^2} \frac{R_2'}{s}; \quad P_{\text{air_gap}} = I_2'^2 \frac{R_2'}{s}$$

$$S_{T_{\text{max}}} = \frac{R_2'}{\sqrt{R_{\text{th}}^2 + (X_{\text{th}} + X_2')^2}}; \quad T_{\text{max}} = \frac{1}{2\omega_s} \frac{V_{\text{th}}^2}{R_{\text{th}} + \sqrt{R_{\text{th}}^2 + (X_{\text{th}} + X_2')^2}}$$

DC MACHINES

$$K_a = \frac{Z_p}{2\pi a}; \quad E_a = K_a \phi \omega; \quad T = K_a \phi I_a; \quad P_{\text{out}} = E_a I_a = T\omega; \quad L_a = p \text{ wound.}$$

OTHERS

$$S = \sqrt{3} V_L I_L; \quad Z_{\text{pu}} = \frac{Z_{\text{ohm}}}{Z_{\text{base}}}; \quad Z_b = \frac{(kV_b)^2}{\text{MVA}_b};$$

$$S_{\text{pu}} = kV_{\text{pu}} kA_{\text{pu}} (\text{no } \sqrt{3}); \quad kA_{\text{pu}} = \frac{\text{MVA}_b}{\sqrt{3} \text{kVA}_b}; \quad Z_{\text{pu}2} = Z_{\text{pu}1} \times \frac{S_{b2}}{S_{b1}} \times \frac{kV_{b1}^2}{kV_{b2}^2}$$